

UNIVERSITY OF VICTORIA

ELEC 250

LINEAR CIRCUITS I

Lab 2 - Phasor Analysis

Instructor:

Dr. Nikitas DIMOPOULOS

Teaching Assistant:

Zhen LIU

Clayton KIHN V00794569
Yves SENECHAL V00213837
Tyler STEPHEN V00812021
A01 - B01

October 14, 2014



1 Object

This lab will study the steady-state responses of an RC and RL circuit when exposed to a purely sinusoidal voltage source. The current response and the phase shift of current relative to voltage will be calculated and compared with measured values.

2 Results

An Agilent 33220A signal generator was used to create the sinusoidal voltage source used in this lab. A peak-to-peak voltage of 10.5 V was used for both circuits. Different frequencies were used in each section and is discussed further in sections 2.1 and 2.2.

An Agilent DSOX-2012A oscilloscope was used to analyze the maximal current and phase shift.

2.1 RC Circuit

The circuit was connected as show in figure 1 using selectable capacitor and resistor boxes provided in the lab. A 5 nF capacitor was used in the circuit. A sinusoidal voltage source with a frequency 10 kHz was applied to the circuit.

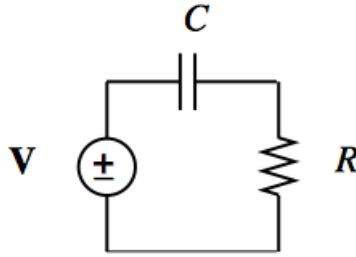


Figure 1: The RC circuit used in the lab

The expected phase shift, with current leading voltage, is given by equation (1), where $\omega = 2\pi f$. The expected maximum current is given by equation (2).

$$\tan \theta = \left(\frac{1}{\omega RC} \right) \quad (1)$$

$$I_{max} = \frac{V_{max}}{\sqrt{R^2 + \left(\frac{1}{C\omega}\right)^2}} \quad (2)$$

The calculated and measured values of the current (I) and phase shift (θ) are summarized in table 1.

R (k Ω)	Calculated		Measured	
	I (mA)	θ ($^\circ$)	I (mA)	θ ($^\circ$)
1	3.15	72.56	3.10	70.89
5	1.77	32.48	1.76	31.12
10	1.00	17.67	0.98	14.89

Table 1: Calculated and measured values in the RC circuit

2.2 RL Circuit

The circuit was connected as shown in figure 2. The resistor box was reused and discrete inductors were obtained from the lab (see tables 2 and 3). The frequency of the voltage source was set to 500 kHz.

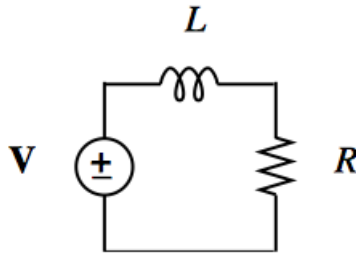


Figure 2: The RL circuit used in the lab

The expected phase shift of current with respect to voltage is given by equation (3). The negative sign indicates that voltage will lead current. The expected maximum current is given by equation (4).

$$\tan \theta = \left(\frac{-\omega L}{R} \right) \quad (3)$$

$$I_{max} = \frac{V_{max}}{\sqrt{R^2 + L^2 \omega^2}} \quad (4)$$

Calculated values for each pairing of resistor and inductor is summarized in table 2. Measured results are presented in table 3.

R (k Ω)	1 μ H		220 μ H		470 μ H		1000 μ H	
	I (mA)	θ ($^\circ$)	I (mA)	θ ($^\circ$)	I (mA)	θ ($^\circ$)	I (mA)	θ ($^\circ$)
1	10.50	-0.18	8.64	-34.65	5.89	-55.89	3.18	-72.34
5	2.10	-0.04	2.08	-7.87	2.01	-16.45	1.78	-32.14
10	1.05	-0.02	1.05	-3.95	1.04	-8.40	1.00	-17.44

Table 2: Calculated values in the RL circuit

R (k Ω)	1 μ H		220 μ H		470 μ H		1000 μ H	
	I (mA)	θ ($^\circ$)	I (mA)	θ ($^\circ$)	I (mA)	θ ($^\circ$)	I (mA)	θ ($^\circ$)
1	3.00	-84	9.00	-36	6.00	-63	3.18	-82
5	2.46	-61	2.34	-9	2.58	-25	2.66	-58
10	2.01	-51	1.17	-5	1.41	-13	2.01	-42

Table 3: Measured values in the RL circuit

3 Discussion and Conclusion

The RC series circuit performed as expected. The current was positively phase shifted and lead the voltage. The current decreased due to the impedance introduced by the capacitor. The current and the phase shift measured lower than calculated, which could be explained by added resistance within the circuit. Equations (1) and (2) show that a higher resistance would yield both a lower current and a smaller phase shift. The slight variation between calculated and measured values indicates that this added resistance was minimal.

The RL series circuit performed as expected for the 220 μ H with the 470 μ H and 1 mH with only slight variation. In these three cases, the current was negatively phase shifted and voltage lead current. The current decreased due to the impedance introduced by the inductor. The RL circuit yielded a higher current and bigger phase shift than expected, which could be explained by added resistance within the circuit. Contrary to RC circuit, equations (3) and (4) show that a higher resistance within an RL circuit would yield both a higher current and a bigger phase shift.

The 1 μ H inductor circuit, whether combined with the 1 k Ω , 5 k Ω , or the 10 k Ω resistors, provided results that appeared nearest to the values expected of a 1 mH inductor. This part of the experiment was performed with two different 1 μ H inductors that yielded similar results. Possible justification for these discrepancies include: (a) *faulty components*: in this case, both 1 μ H inductors must be faulty; or, (b) *mislabeled inductors*: the difference between the symbol for mH and μ H may be difficult to differentiate when handwritten on heat shrink.

Connection points, wires, measuring devices (oscilloscope), and heat contributed to the added resistance observed in the circuit. Also the discrepancies between measured and calculated values could be attributed to the use of non-ideal components; each circuit component adds a degree of uncertainty. However, capacitors are more predictable than inductors when connected to a circuit. This could be due to a by-product of heat produced within an inductor, or the improved accuracy of mass-producing capacitors versus inductors.