

UNIVERSITY OF VICTORIA

ELEC 250

LINEAR CIRCUITS I

---

## Lab 3 - Transient Analysis

---

*Instructor:*

Dr. Nikitas DIMOPOULOS

*Teaching Assistant:*

Zhen LIU

Clayton KIHN V00794569  
Yves SENECHAL V00213837  
Tyler STEPHEN V00812021  
A01 - B01

November 2, 2014



**University  
of Victoria**

# 1 Object

This lab will study the transient response of an RC and an RL circuit.

## 2 Results

An Agilent 33220A signal generator was used to create the momentary single pulse excitation, while an Agilent DSOX-2012A oscilloscope was used to analyze transient responses of the RC and RL circuits.

### 2.1 RC Circuit

The circuit was constructed as shown in Figure ?? and excited using a  $5\text{ V}_{pp}$  single pulse source for a duration of 5ms.

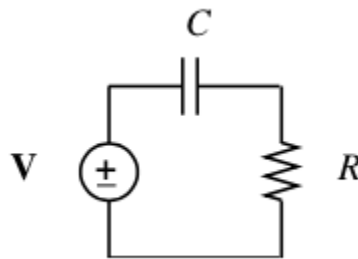


Figure 1: RC circuit driven by a source.  $R = 4.7\text{ k}\Omega$  and  $C = 100\text{ nF}$ .

Measured values of the change in voltage across the capacitor and resistor in this circuit were recorded on the oscilloscope and are displayed in Figure ?. In order to measure  $v_R$ , it was necessary to switch the order of  $R$  and  $C$ .

The expected value of the time constant  $\tau$  is given by

$$\tau = RC \tag{1}$$

Using (?), the expected value of  $\tau$  is  $480\mu\text{s}$ . By measuring the time it took for  $v_C$  to decay to 37.25% of its original value in Figure ?.c,  $\tau$  was determined to be  $480\mu\text{s}$ .

## 2.2 RL Circuit

The circuit was constructed as shown in Figure ?? and excited using a  $5\text{ V}_{pp}$  single pulse source for a duration of  $23.53\mu\text{s}$ .

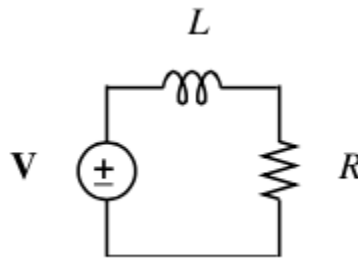


Figure 2: RL circuit driven by a source.  $R = 680\ \Omega$  and  $L = 1.00\text{ mH}$ .

Measured values of the change in voltage across the inductor and resistor in this circuit were recorded on the oscilloscope and are displayed in Figure ?. In order to measure  $v_R$ , it was necessary to switch the order of  $R$  and  $L$ .


The expected value of the time constant  $\tau$  is given by

$$\tau = \frac{L}{R} \quad (2)$$


Using (?), the expected value of  $\tau$  is  $1.4\mu\text{s}$ . By measuring the time it took for  $v_R$  to rise to 67.75% of its final val in Figure ?.c,  $\tau$  was determined to be  $1.4\mu\text{s}$ . The time for  $v_L$  to decay to 37.25% of its original value in Figure ?.d yielded a  $\tau$  of  $1.34\mu\text{s}$ .
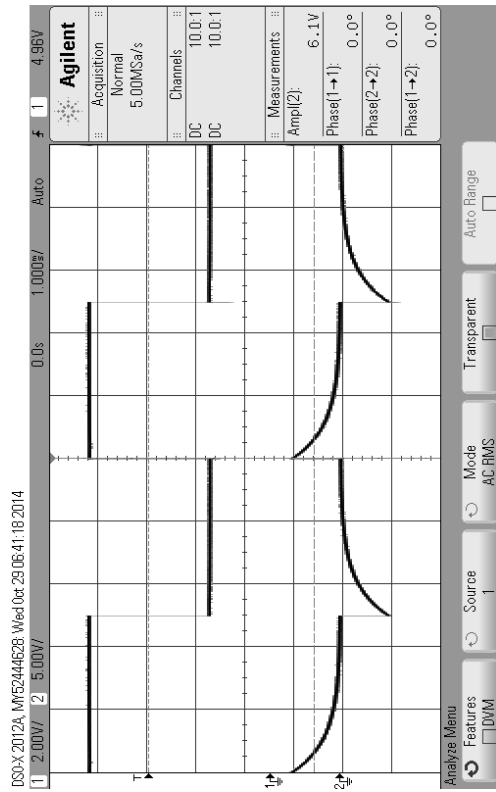
## 3 Discussion and Conclusion


The discussion and conclusion should answer the questions that are posed in the procedure section of the experiment. Any special observations made by the student can be recorded here.



(a)  $v_s$  and  $v_R$

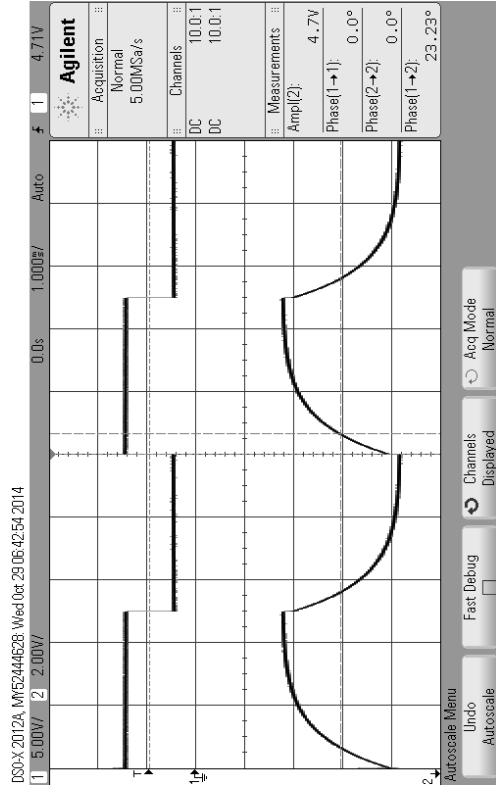


(b)  $v_s$  and  $v_C$

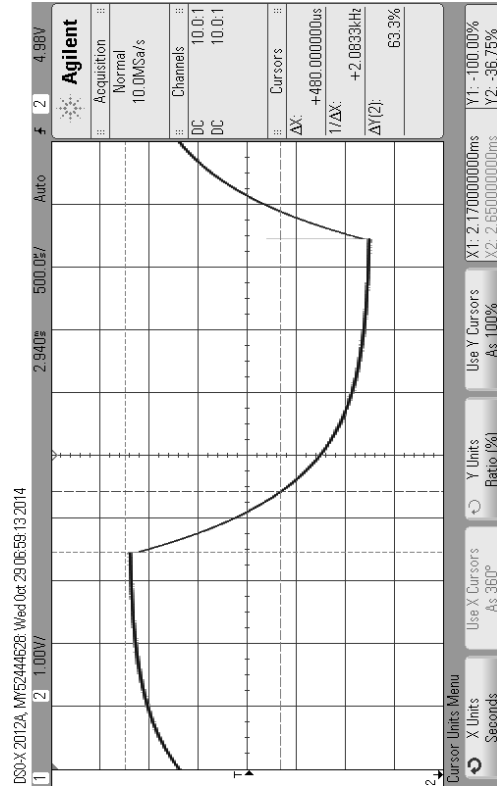


(c) Decay of  $v_C$  used to find  $\tau$


Figure 3: Transient response of the RC circuit

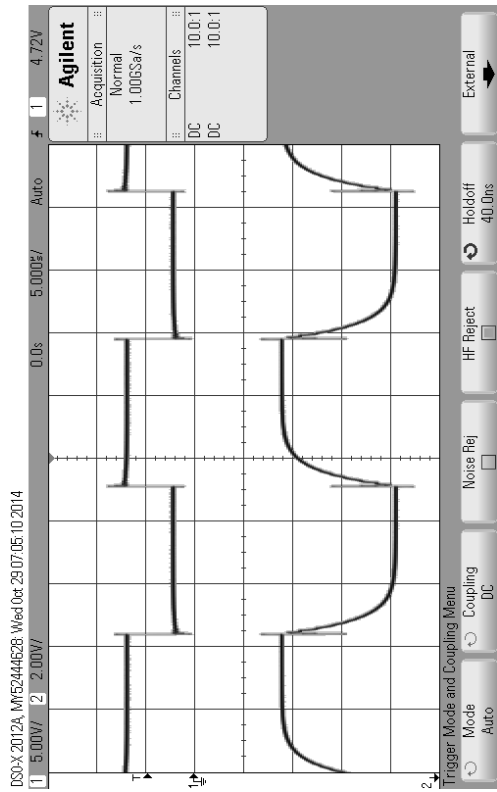


(a)  $v_s$  and  $v_R$

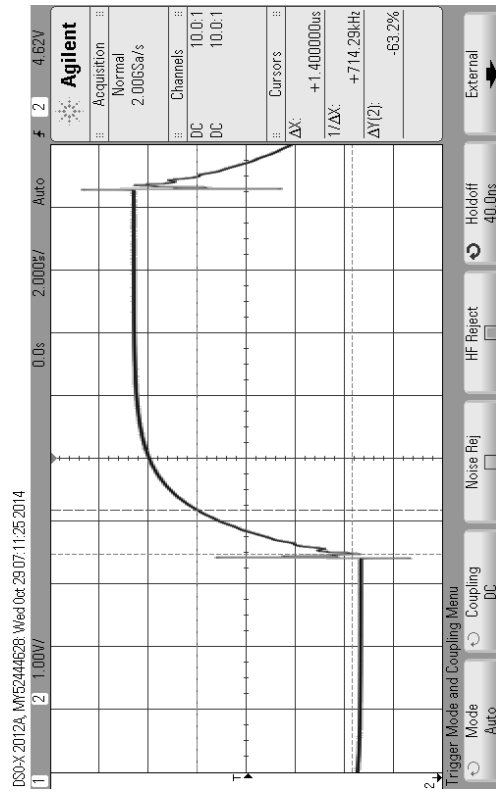

(c) Rise of  $v_R$  used to find  $\tau$

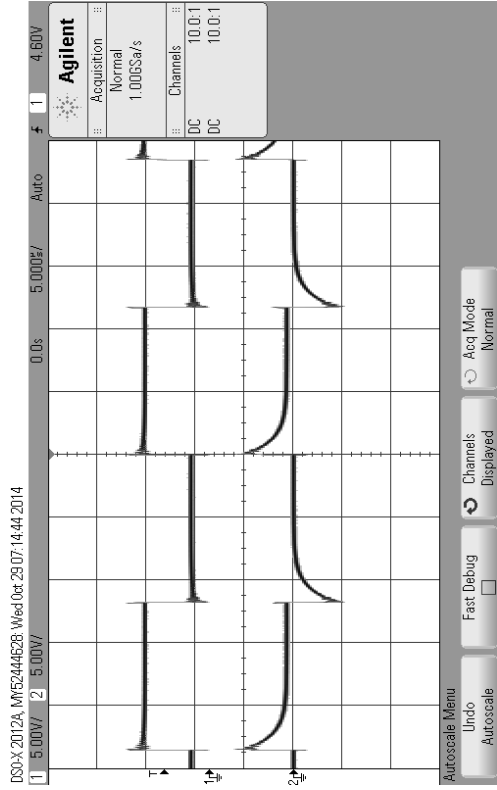

(b)  $v_s$  and  $v_L$

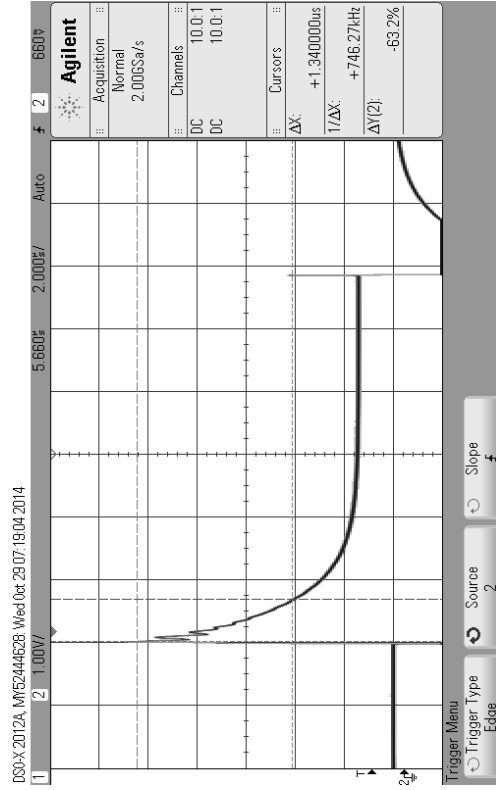

(d) Decay of  $v_L$  used to find  $\tau$

Figure 4: Transient response of the RL circuit